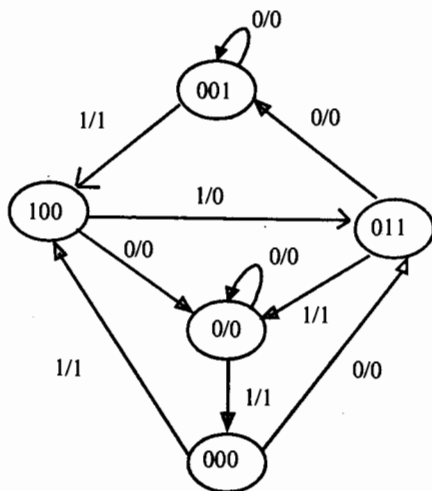


5. Answer any two parts : (10×2=20)

(a) A sequential circuit has one input and one output. The state diagram is shown in following figure :



Design the sequential circuit with T flip-flops.

(b) A sequential circuit has four flip-flops A, B, C, D and an input x. It is described by following state equations :

$$A(t+1) = (C'D' + C'D)x + (CD + C'D')x'$$

$$B(t+1) = A$$

$$C(t+1) = B$$

$$D(t+1) = C.$$

- (i) Obtain the sequence of states when $x = 1$ starting from ABCD = 0001.
 - (ii) Obtain the sequence of states when $x = 0$ starting from ABCD = 0000.
- (c) Write short notes on any two of the following :
- (i) Asynchronous sequential logic versus Synchronous sequential logic.
 - (ii) Hazards in combinational and sequential circuits.
 - (iii) State reduction in sequential circuits.

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0109 Roll No.

--	--	--	--	--	--	--	--	--	--



COMPUTER GEEK
compgeek.co.in

B. Tech.

(SEM. III) THEORY EXAMINATION 2011-12

DIGITAL LOGIC DESIGN

Time : 3 Hours

Total Marks : 100

Note :- Answer all questions.

1. Answer any four parts : (5×4=20)
 - (a) How can functionalities of the OR gate be realized using only NAND gates ?
 - (b) Simplify following boolean expressions :
 - (i) $A + A'B + A'B'C + A'B'C'D + A'B'C'D'E + A'B'C'D'E'F$
 - (ii) $D(A'+B) + B'(C+AD)$
 - (c) What is Hamming Code ? How it is used for detecting and correcting errors ? Explain with the help of suitable example.
 - (d) Express the following boolean function F in a sum of minterms and a product of maxterms :

$$F(x, y, z) = (xy + z)(y + xz)$$
 - (e) Simplify the boolean function G using the don't care conditions d using Karnaugh map :

$$G = A'B'D + A'CD + A'BC$$

$$d = A'BC'D + ACD + AB'D'$$



COMPUTER GEEK
compgeek.co.in

- (f) (i) Convert the decimal number 225.225 to binary number.
- (ii) Perform following arithmetic operation in binary using signed 2' complement representation :
 $(-42) - (-13)$

2. Answer any **four** parts : (5×4=20)

- (a) Design a logic circuit whose output is 1 only when a majority of inputs A, B, C are 0.
- (b) Implement a full subtractor with two half subtractors and an OR gate.
- (c) Implement the following boolean function F using three half adder circuits:
 $F(A, B, C) = A \oplus B \oplus C$.
- (d) Design a combinational circuit that compares the magnitude of two 4 bit numbers and its output indicates whether $A > B$, $A = B$ or $A < B$.
- (e) What is multiplexer ? Give implementation of a full adder circuit using 4×1 multiplexers.
- (f) What is priority encoder ? Explain with the help of suitable example.

3. Answer any **two** parts : (10×2=20)

- (a) (i) What is flip-flop ? Draw the logic diagram and give the characteristic table of J K flip-flop.
- (ii) Explain the race condition in context of RS flip-flop.



- (b) Design a binary counter using J K flip-flops having the following repeated sequences :

0, 4, 2, 1, 6

- (c) What is shift register ? Draw diagram of a 4-bit binary ripple down counter using flip flops that trigger on negative edge transition. Also draw a timing diagram of the counter.

4. Answer any **two** parts : (10×2=20)

- (a) (i) A certain memory has a capacity of $4 \text{ K} \times 8$. How many data input and data output lines does it have ? How many address lines does it have ? What is its capacity in Bytes ?
- (ii) Discuss the following types of ROM, PROM, EPROM, EEPROM.
- (b) (i) Design a 16×8 memory using 16×4 memory units.
- (ii) Differentiate between programmable array logic (PAL) and programmable logic assays (PLA).
- (c) (i) Draw the logic diagram of 4 input multiplexer. Further show how 4-input multiplexer can be realized using 2-input multiplexers.
- (ii) Draw the logic diagram of one line to 8-line demultiplexer.