



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 995302

Roll No.

--	--	--	--	--	--	--	--	--	--



B.Tech.
(SEM. III) (ODD SEM.) THEORY
EXAMINATION, 2014-15
DIGITAL DESIGN

Time : 3 Hours]

[Total Marks : 100

Note: Attempt all Sections. Instruction for each question is given there.

Section – A

1. Attempt ALL questions. 2x10=20
- (a) Convert the following: $(62.72)_8 = ()_{16}$
- (b) Represent the decimal number 6 in 84-2-1 code, excess-3 code & BCD code.
- (c) Minimize the following expression using k-map:
 $Y(A,B,C) = \sum(1,2,6,7) + d(0,5)$
- (d) Explain state assignment.
- (e) Draw the JK flip-flop using NAND gate.
- (f) Implement the following Boolean function by using multiplexer. $F(P,Q,R,S) = \sum m(0,5,7,8,9,10,11,12,13,15)$
- (g) How many address lines are needed to operate a 2K x 8 ROM?



4. Attempt any TWO Questions.

2x5=10

- a). Design a full subtractor circuit with a decoder and two OR Gates.
- b). What is priority encoder? Explain with the help of suitable example.
- c). Design a combinational logic circuit with three input variables that will produce logic 1 output when more than one input variables are logic 0.

5. Attempt any ONE Question.

10x1=10

- a). Draw neat diagram of Universal shift register. Explanation not required.
- b). Draw Mod 10/BCD counter. Also draw state diagram for it. Explanation not required.

6. Attempt any ONE Question.

10x1=10

- a). Explain Random Access Memory (RAM). Also draw block diagram of 4x4 RAM.
- b). Reduce the state diagram shown in figure-1.

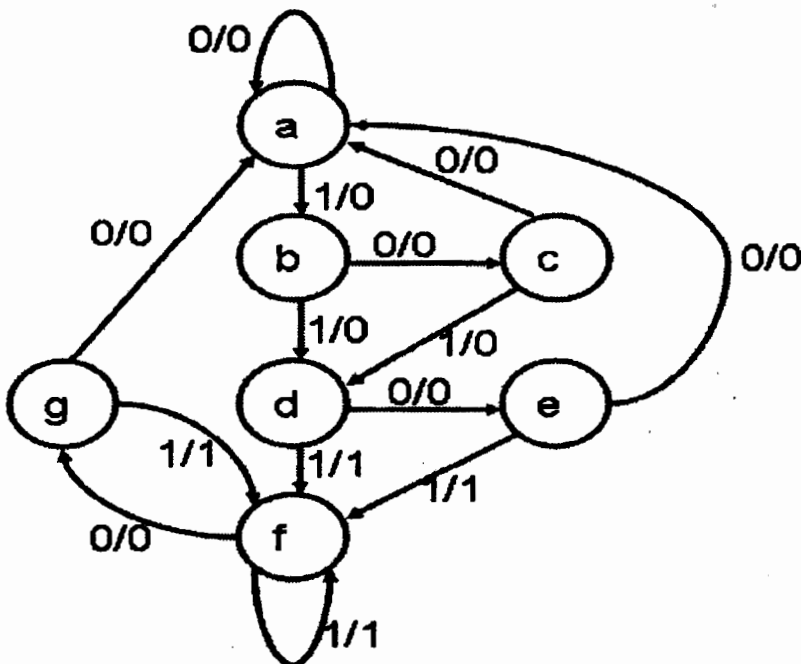


Figure.-1
3

7. Attempt any ONE Question.

10x1=10

- a). Explain the design procedure of asynchronous sequential circuit with suitable example.
- b). Explain race free state assignment in asynchronous sequential circuit with suitable example. Also explain Critical Race and Noncritical Race.

